

Figure 2. Typical circuit.

The user determines the diode and resistor selection according to the maximum current required for capacitor charging. Contact the manufacturer of the capacitor or check the capacitor data sheet for charging-current limits.

Charging-Current Calculations

The maximum charging current can be calculated as follows: assume that a system power supply of 3.3V is applied to V_{CC} , and that the trickle charger has been enabled with no diode and a 2k Ω resistor. The maximum current, when the capacitor voltage is zero, would be calculated as:

$$\begin{aligned}
 I_{MAX} &= (V_{CC} - \text{diode drop})/R2 \\
 &= (3.3V - 0V)/R2 \\
 &\approx (3.3V - 0V)/2k\Omega \\
 &\approx 1.65mA
 \end{aligned}$$

As the voltage on V_{BACKUP} increases, the charging current decreases.

Calculating Backup Time

Now we need to determine how large the capacitor needs to be. Given the desired backup time, we need to know several other parameters: the starting and ending voltage on the capacitor, the current draw from the capacitor, and the capacitor size.

If we assume that the RTC draws a constant current while running from V_{BACKUP} , then calculating the worst-case backup time in hours would use the formula:

$$[C(V_{BACKUPSTART} - V_{BACKUPMIN})/I_{BACKUPMAX}]/3600$$

Where:

C is the capacitor value in farads

$V_{BACKUPSTART}$ is the initial voltage in volts (the voltage applied to V_{CC} , less the voltage drop from the diodes, if any, used in the charging circuit)

$V_{BACKUPMIN}$ is the ending voltage in volts (the minimum oscillator operating voltage)

$I_{BACKUPMAX}$ is the maximum data sheet V_{BACKUP} current in amps

Given that $C = 0.2\text{F}$, $V_{\text{BACKUPSTART}} = 3.3\text{V}$, $V_{\text{BACKUPMIN}} = 1.3\text{V}$, and $I_{\text{BACKUPMAX}} = 1000\text{nA}$, then:

$$\text{Hours} = [0.2(3.3 - 1.3)/(1e - 6)]/3600 = [0.2(2.0)/(1e - 6)]/3600 = 111.1$$

If we want to know what the typical backup time should be, we would substitute the I_{BACKUP} typical value ($I_{\text{BACKUPTYP}}$) for I_{BACKUP} maximum ($I_{\text{BACKUPMAX}}$).

Therefore, if $V_{\text{BACKUPTYP}}$ is 3.3V (typ) and $I_{\text{BACKUPTYP}}$ is 600nA (typ), then:

$$\text{Hours} = [0.2(3.3 - 1.3)/(600e - 9)]/3600 = [0.2(2.0)(600e - 9)]/3600 = 185.2$$

These calculations assume that I_{BACKUP} is constant, regardless of the voltage on V_{BACKUP} . The oscillator on Maxim RTCs tends to act more like a resistor, so that backup current tends to decrease with the backup voltage. It should, therefore, be possible to calculate a more realistic backup time.

From basic electronics, the formula to determine the voltage across a capacitor at any given time (for the discharge circuit in **Figure 3**) is:

$$V(t) = E(e^{-\tau/RC})$$

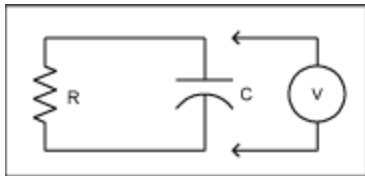


Figure 3. Discharge circuit.

Where:

τ is the time in seconds

E is the initial voltage in volts

V is the ending voltage in volts

R is the resistive load in ohms

C is the capacitor value in farads

Rearranging the equation to solve for t , we get:

$$-\ln(V/E)(RC) = t$$

From the RTC data sheet, we can get the minimum oscillator operating voltage as well as the maximum V_{BACKUP} current ($I_{\text{BACKUPMAX}}$). To estimate the load resistance, R , we divide the data sheet $V_{\text{BACKUPMAX}}$ by $I_{\text{BACKUPMAX}}$ (because the worse-case current occurs at the maximum input voltage). For this example, $V_{\text{BACKUPMAX}}$ is 3.7V and $I_{\text{BACKUPMAX}}$ is 1000nA, or $3.7/1e-6$ or 3,700,000 Ω . Assuming that the capacitor value is 0.2F and has been charged to 3.3V, that the $I_{\text{BACKUPMAX}}$ is 1000nA, and that the minimum oscillator operating voltage is 1.3V, the backup time would be calculated as:

$$\begin{aligned} &-\ln(V_{\text{BACKUPMIN}}/V_{\text{BACKUPMAX}})[(V_{\text{BACKUPMAX}}/I_{\text{BACKUPMAX}}) \times C] = \\ &-\ln(1.3/3.3)(3,700,000 \times 0.2) = \\ &689,353\text{s} \text{ (191.5hrs)} \end{aligned}$$

By changing the value of C , the estimated operating time while running from the backup capacitor can be determined.

These calculations can be done using the [on-line calculator](#). This Supercapacitor Calculator implements the three equations shown above.

Related Parts		
DS1302	Trickle-Charge Timekeeping Chip	Free Samples
DS1305	Serial Alarm Real-Time Clock	Free Samples
DS1306	Serial Alarm Real-Time Clock	Free Samples
DS1339	I ² C Serial Real-Time Clock	Free Samples
DS1339A	Low-Current, I ² C, Serial Real-Time Clock	Free Samples
DS1340	I ² C RTC with Trickle Charger	Free Samples
DS1343	Low-Current SPI/3-Wire RTCs	Free Samples
DS1344	Low-Current SPI/3-Wire RTCs	Free Samples
DS1374	I ² C, 32-Bit Binary Counter Watchdog RTC with Trickle Charger and Reset Input/Output	Free Samples
DS1388	I ² C RTC/Supervisor with Trickle Charger and 512 Bytes EEPROM	Free Samples
DS1390	Low-Voltage SPI/3-Wire RTCs with Trickle Charger	Free Samples
DS1391	Low-Voltage SPI/3-Wire RTCs with Trickle Charger	Free Samples
DS1392	Low-Voltage SPI/3-Wire RTCs with Trickle Charger	Free Samples
DS1393	Low-Voltage SPI/3-Wire RTCs with Trickle Charger	Free Samples
DS1394	Low-Voltage SPI/3-Wire RTCs with Trickle Charger	Free Samples
DS1672	I ² C 32-Bit Binary Counter RTC	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 3517: <http://www.maximintegrated.com/an3517>

APPLICATION NOTE 3517, AN3517, AN 3517, APP3517, Appnote3517, Appnote 3517

© 2013 Maxim Integrated Products, Inc.

Additional Legal Notices: <http://www.maximintegrated.com/legal>