



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 1016

Keywords: inverting, dc-dc regulator, autotransformer, switching regulator, ICs, integrated circuit

APPLICATION NOTE 1016

# Autotransformer Regulator Inverts 12V to -12V

Jul 09, 1998

*Abstract: The autotransformer provides an alternative means of extending the output voltage range of an inverting DC-DC regulator besides using an external MOSFET or a flyback transformer. With an autotransformer, the input-output voltage can be extended beyond the specification limit of the integrated circuit (IC).*

In **Figure 1**, a dc-dc regulator with internal switching MOSFET inverts 12V to produce an output of 200mA at -12V. The IC is a high-efficiency device whose low quiescent current (120 $\mu$ A maximum) is achieved with a CMOS process that limits the absolute maximum voltage to 21V (input to output). Thus, to avoid 24V across its terminals, the IC must isolate itself from the inductor-flyback voltage by driving either an external switch in a non-bootstrapped configuration, or an internal switch in a flyback-transformer configuration.

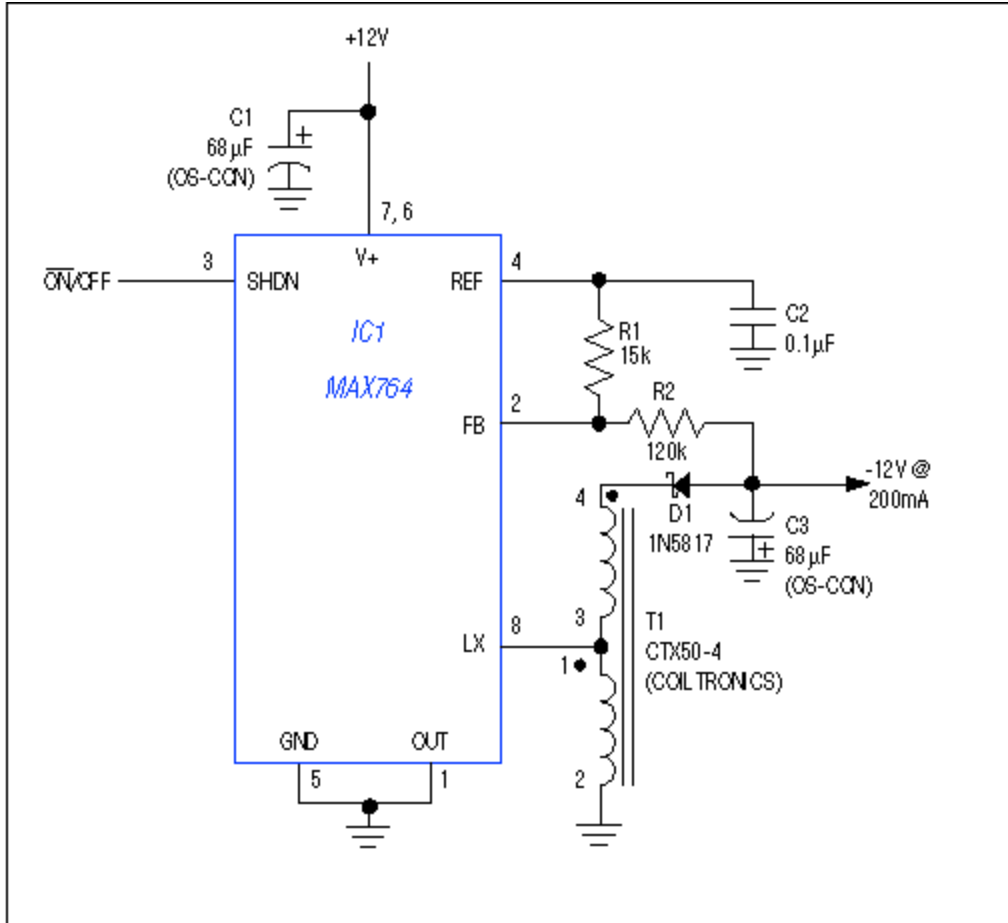


Figure 1. Autotransformer T1 limits the voltage across IC1, allowing use of a high-efficiency chip (with 21V absolute-maximum voltage) in this inverting dc-dc regulator.

Autotransformer T1 (a center-tapped inductor with 1:1 turns ratio) offers a design alternative. In the circuit shown, LX flies back to  $1/2V_{OUT}$  plus a diode drop, or approximately -6V. V+ remains at 12V, producing an 18V maximum between V+ and LX that is well within the 21V limit.

Because IC1 drives the gate of its internal MOSFET between the V+ and OUT voltages, you normally connect OUT to  $V_{OUT}$  to ensure sufficient gate drive (in a typical application, the chip inverts 5V to -5V). In this circuit the 12V input provides adequate gate drive, so OUT is connected to ground.

#### Related Parts

[MAX764](#)

-5V/-12V/-15V or Adjustable, High-Efficiency, Low- $I_Q$  DC-DC Inverters

[Free Samples](#)

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 1016: <http://www.maximintegrated.com/an1016>

APPLICATION NOTE 1016, AN1016, AN 1016, APP1016, Appnote1016, Appnote 1016

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>